

PROJECT REPORT

- CAR BATTERY
CHARGER
- POWER SUPPLY



Table Of Content

03 Overview and goals

04 Our Team

05 Calculations of battery charger

06 Components of battery charger

07 Simulation Result of battery charger

08 PCB Design and Arduino Code

09 Power Supply

10 Calculations of power supply

11 Components of power supply

12 Simulation Result of Power supply and the full connections

13 PCB Design

Overview

Making a device using the Boost converter to charge the car battery

Goals

- **Goal 1**

Using the Boost converter to raise the voltage from 5V input source, i.e. DC Adapter, to a voltage suitable for charging a car battery

- **Goal 2**

Designing a power supply by adding some modifications to the Boost Converter

Calculations

$$\therefore V_{in} = 5 \text{ V} \quad V_o = 14.4 \text{ V} \quad I_o = 10 \text{ A}$$

$$\therefore R_l = V_o / I_o = 1.44 \Omega$$

$$\therefore \text{For the boost converter} \rightarrow \therefore V_o / V_{in} = 1 / (1 - D)$$

$$\therefore D = 0.653$$

(in percentage = 65.3 %)

$$\therefore I_c = C * dV/dT$$

$$\therefore V_l = L * dI_l/dT$$

$$\therefore \Delta V_o = (V_o * D) / R_o * C * F_s$$

$$\therefore \Delta I_L = (V_{in} * D) / (L * F_s)$$

$$\therefore \text{Let, } \Delta I_L = 30\% I_L \text{ \& } \Delta V_o = 1\% V_o \text{ \& } F_s = 100 \text{ KHz}$$

$$\therefore \text{Assume that the voltage is 14.4V and the current is 10A to take the losses in consideration.}$$

$$\therefore I_L = \frac{V_o}{D' * R} = \frac{14.4}{0.347 * 1.44} = 28.82 \text{ A} \rightarrow \Delta I_L = 0.3 * 28.82 = 0.8645$$

$$\therefore 0.8645 = \frac{5 * 0.653}{L * 100 \text{ KHz}} \rightarrow \therefore L = 3.77 \mu\text{H}$$

take the standard value = 3.3 μH

$$\therefore 0.144 = \frac{14.4 * 0.653}{1.44 * C * 100 \text{ KHz}} \rightarrow \therefore C = 453 \mu\text{F}$$

take the standard value = 470 μF

Components

Element	Value
Resistor	1.44Ω
Inductor	3.3 uH
Capacitor	470 uF

- MOSFET “IRFZ44N”**




QUICK REFERENCE DATA

SYMBOL	PARAMETER	MAX.	UNIT
V_{DS}	Drain-source voltage	55	V
I_D	Drain current (DC)	49	A
P_{tot}	Total power dissipation	110	W
T_j	Junction temperature	175	°C
$R_{DS(ON)}$	Drain-source on-state resistance $V_{GS} = 10\text{ V}$	22	mΩ


- Diode “1N5822”**

	Symbols	1N 5820	1N 5821	1N 5822	Units
Maximum repetitive peak reverse voltage	V_{RRM}	20	30	40	Volts
Maximum RMS voltage	V_{RMS}	14	21	28	Volts
Maximum DC blocking voltage	V_{DC}	20	30	40	Volts
Maximum average forward rectified current 0.375"(9.5mm)lead length at $T_L=95^\circ\text{C}$	$I(AV)$	3.0			Amps
Peak forward surge current 8.3ms single half sine-wave superimposed on rated load (JEDEC method) at $T_L=75^\circ\text{C}$	I_{FSM}	80.0			Amps
Maximum instantaneous forward voltage at 3.0 A(Note 1)	V_F	0.475	0.500	0.525	Volts
Maximum instantaneous forward voltage at 9.4 A(Note 1)	V_F	0.850	0.900	0.950	Volts


Simulation result

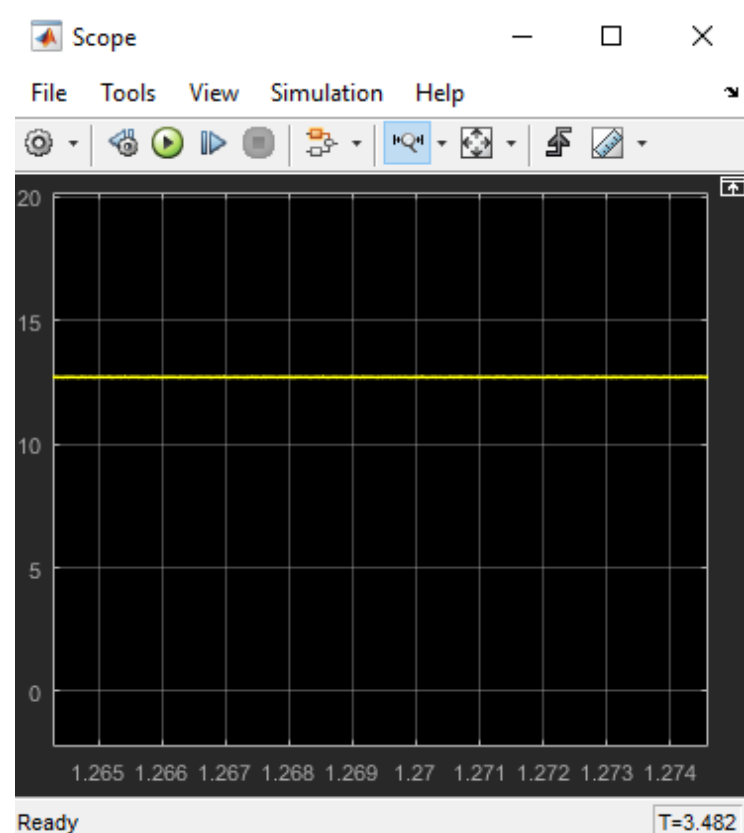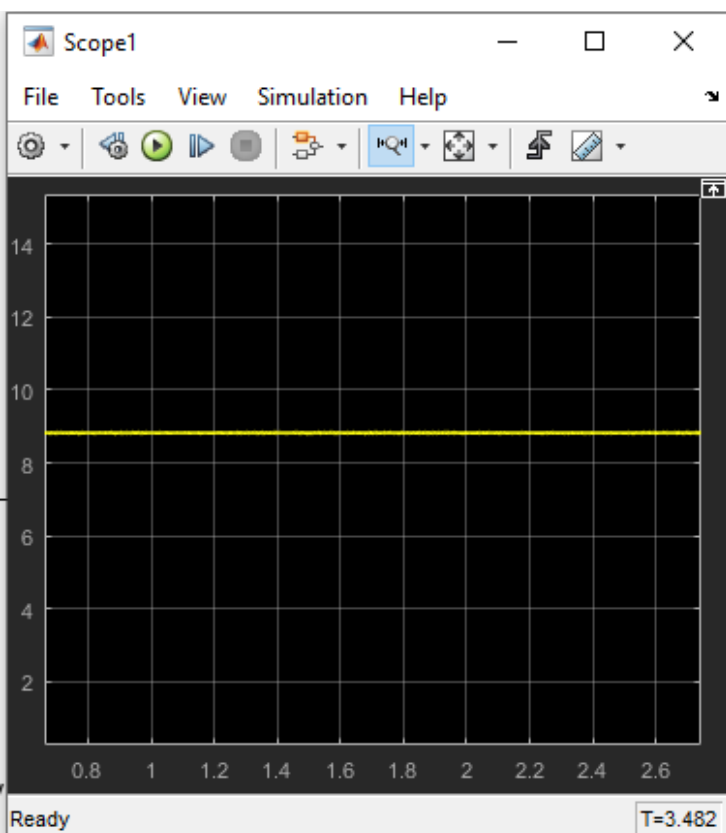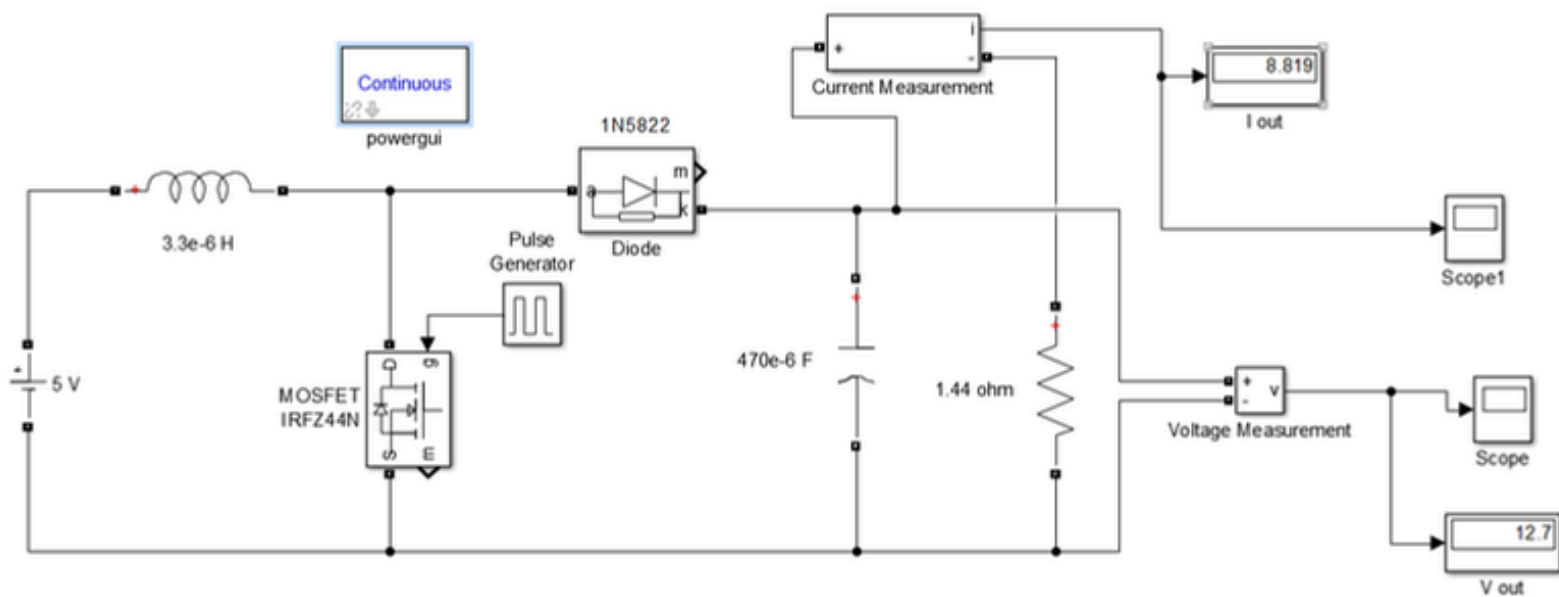

PCB Design

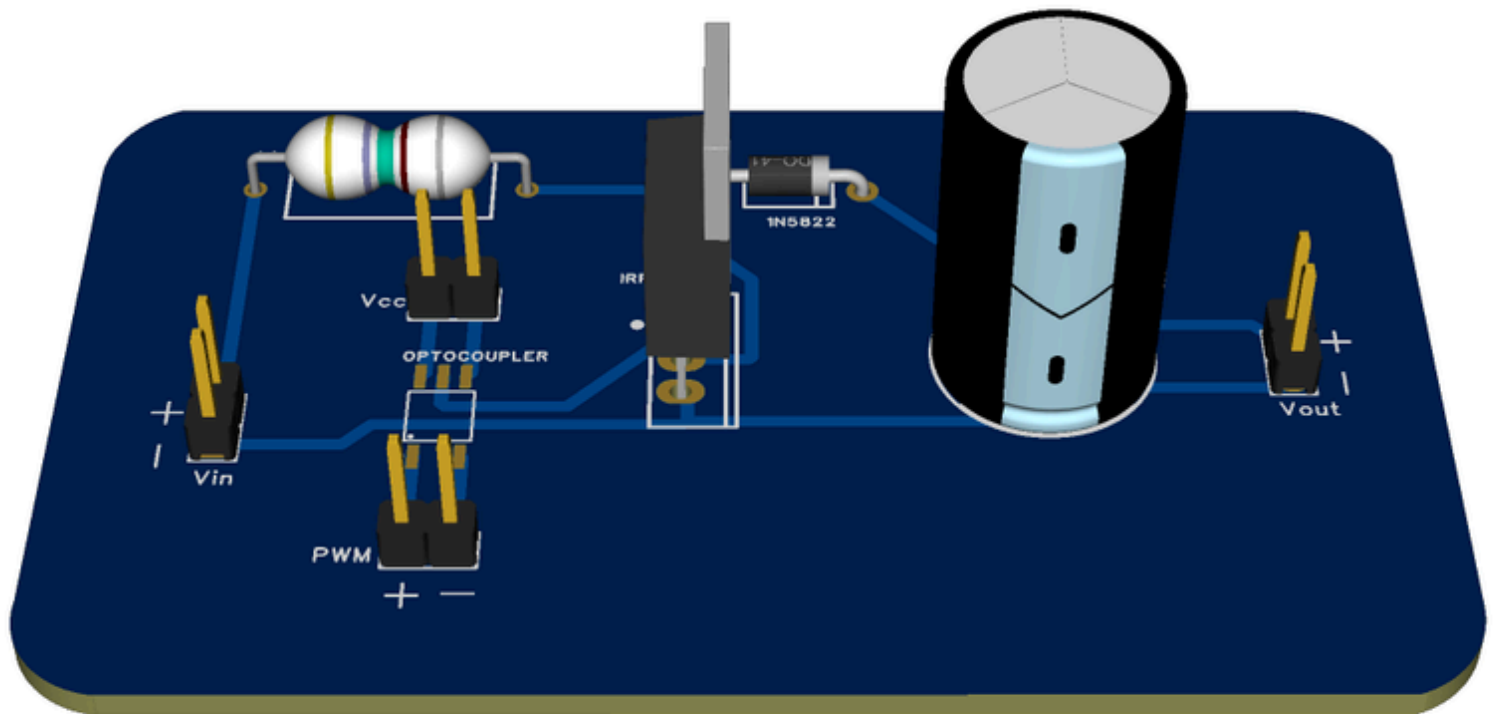

Arduino Code

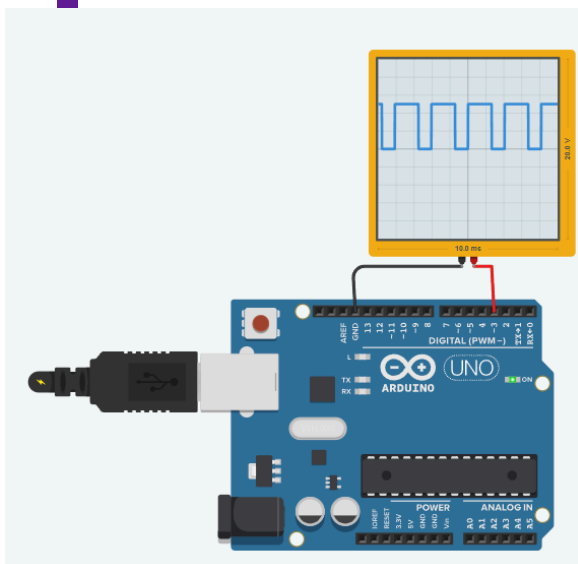

```
3 void setup()
4 {
5     pinMode(3, OUTPUT);
6 }
7
8 void loop()
9 {
10    analogWrite(3, 0.653*255);
11    while (true);
12 }
```

Power Supply

We can obtain a power supply by using the output voltage of the previous circuit as an input to another circuit.


The new circuit provides two output ports

1. One of them is a constant DC voltage equals to the input voltage “12.7 V”.
2. The other is a DC voltage can be adjusted from 1.2 V to a value approximately equal the input voltage “12.7 in this case” by a variable resistance.

Calculations

$$V_O = V_{REF} \left(1 + \frac{R_2}{R_1} \right) + I_{ADJ} R_2$$
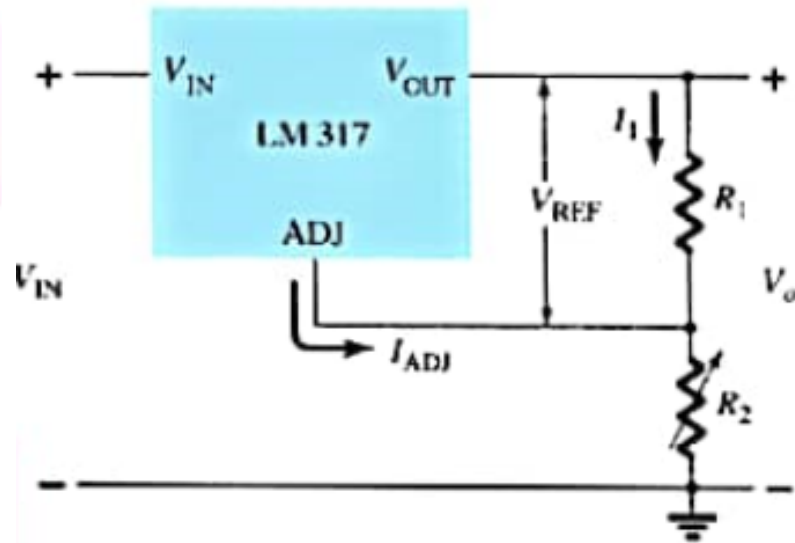
$$I_{ADJ} = 100 \mu A \quad \text{and} \quad V_{REF} = 1.25 V$$



$$\therefore V_O = 1.25 (1 + (R' / R_2))$$

$$\therefore V_O = 12.7 V$$

$$\therefore \text{assume } R = 220 K\Omega$$


$$\therefore 12.7 = 1.25 (1 + (R' / 220 K\Omega)) \longrightarrow \therefore R' = 2.015 K\Omega$$

$$\therefore R' = R_1 // R_3$$

$$\therefore \text{assume } R_1 = 3 K\Omega \longrightarrow \therefore R_3 = 10 K\Omega$$

Components

- MOSFET “LM317”**

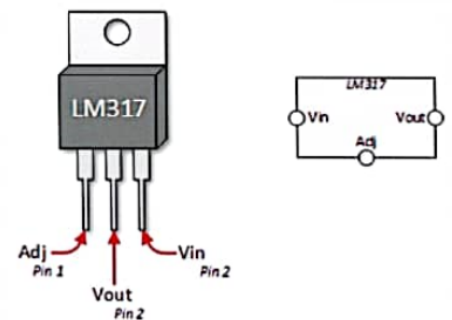

Maximum Ratings

Ratings at 25°C ambient temperature unless otherwise specified.

Parameter	Symbol	Value	Unit
Input-Output Voltage Differential	$V_i - V_o$	40	Vdc
Junction-to-Case Thermal Resistance	$R_{\theta JC}$	3.0 3.0	°C
Power Dissipation, 25°C Case Temperature	P_D	15	W
Operating Junction Temperature Range	T_J	0 to +125	°C
Storage Junction Temperature Range	T_{stg}	-65 to +150	°C

- Diode “1N4007”**


Maximum Ratings and Electrical Characteristics

@ $T_A = 25^\circ\text{C}$ unless otherwise specified


Single phase, half wave, 60Hz, resistive or inductive load.
For capacitive load, derate current by 20%.

Characteristic	Symbol	1N 4001/L	1N 4002/L	1N 4003/L	1N 4004/L	1N 4005/L	1N 4006/L	1N 4007/L	Unit
Peak Repetitive Reverse Voltage	V_{RRM}	50	100	200	400	600	800	1000	V
Working Peak Reverse Voltage	V_{RWM}								
DC Blocking Voltage	V_R								
RMS Reverse Voltage	$V_{R(RMS)}$	35	70	140	280	420	560	700	V
Average Rectified Output Current (Note 1) @ $T_A = 75^\circ\text{C}$	I_o	1.0							A
Non-Repetitive Peak Forward Surge Current 8.3ms single half sine-wave superimposed on rated load (JEDEC Method)	I_{FSM}	30							A
Forward Voltage @ $I_F = 1.0\text{A}$	V_{FM}	1.0							V
Peak Reverse Current @ $T_A = 25^\circ\text{C}$ @ $T_A = 100^\circ\text{C}$	I_{RM}	5.0 50							μA

Simulation Result

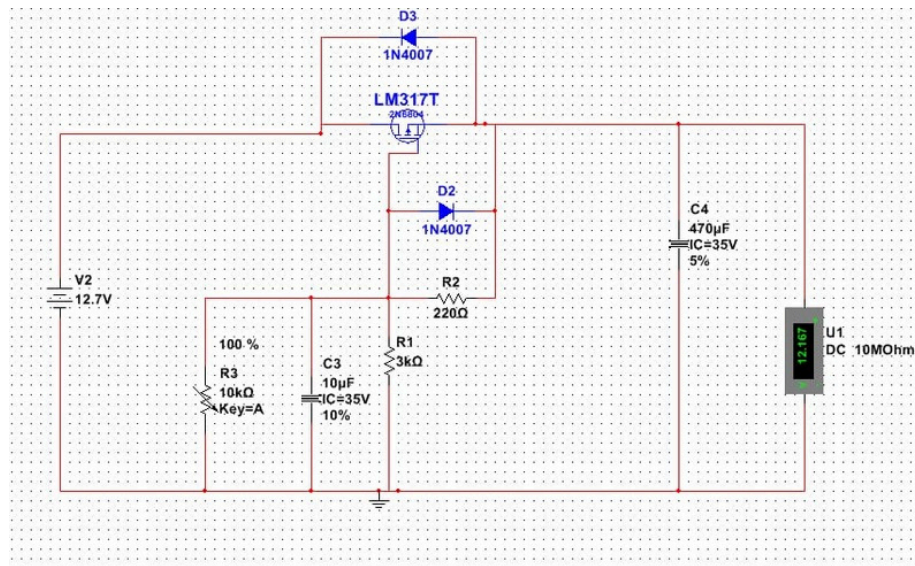

Full Connections

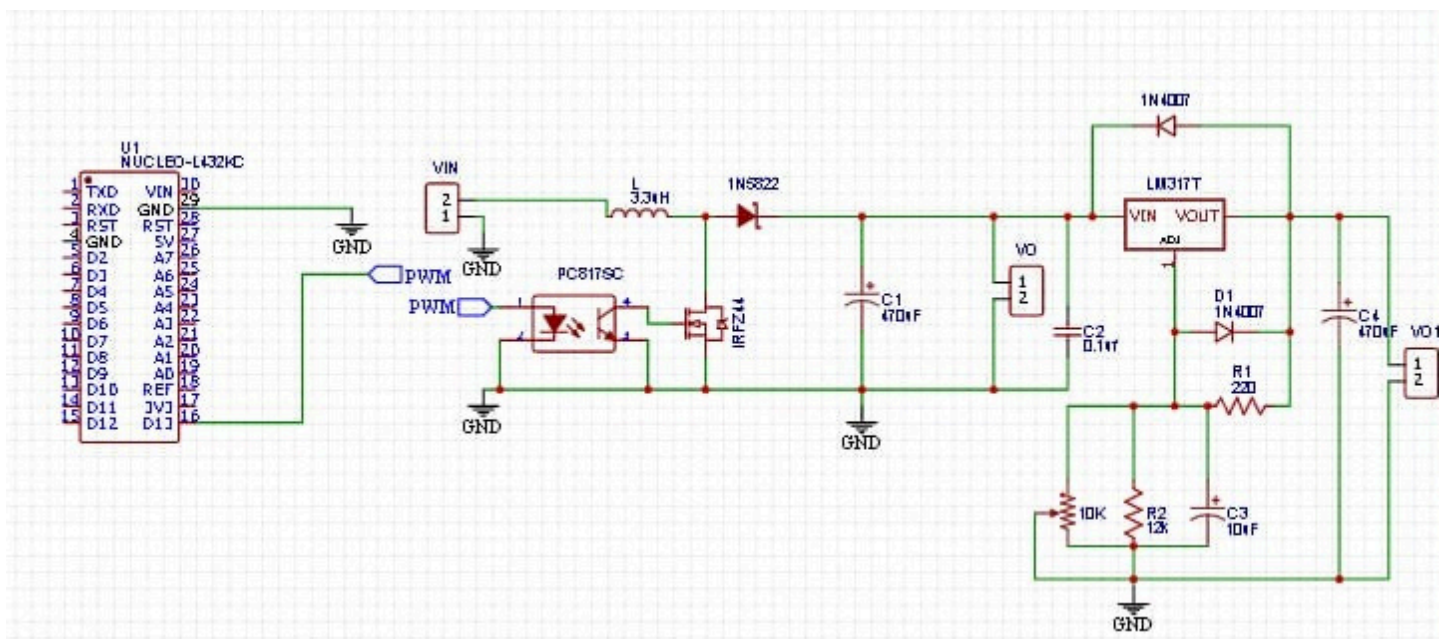

PCB Design

